

10.73.

Puissance dissipée = $R i^2$


1). avec R_{int}



$$U_0 = E - R_{int} i_0 = R i_0$$

$$\Rightarrow i_0 = \frac{E}{R + R_{int}}$$

2). sans R_{int} :

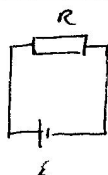

$$U = E = R i$$

$$\Rightarrow i = \frac{E}{R}$$

$$R i_0^2 = 0,9 R i^2$$


$$\frac{i_0}{i} = \sqrt{0,9} = \frac{E}{R + R_{int}} \cdot \frac{R}{E}$$

$$\Rightarrow \sqrt{0,9} (R + R_{int}) = R$$

$$\Rightarrow (\sqrt{0,9} - 1) R = -\sqrt{0,9} \cdot R_{int}$$

$$\Rightarrow \frac{R_{int}}{R} = \frac{\sqrt{0,9} - 1}{-\sqrt{0,9}} \approx \frac{1 - \sqrt{\frac{9}{10}}}{\sqrt{\frac{9}{10}}} = \frac{1 - \frac{3}{\sqrt{10}}}{\frac{3}{\sqrt{10}}} = \frac{\sqrt{10} - 3}{3} = \frac{\sqrt{10}}{3} - 1$$

10.74.

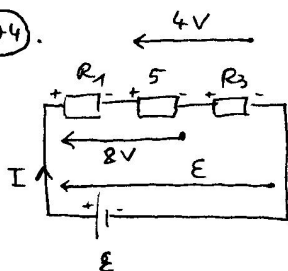

$$\begin{cases} R_1 + R_3 = 17 & (1) \\ (R_1 + 5) \cdot I = 8 & (2) \\ (R_3 + 5) \cdot I = 4 & (3) \\ E = R_{Tot} \cdot I = 22 I & (4) \end{cases} \quad \text{(Lois d'Ohm et de Kirchhoff)}$$

$$\text{de (1): } R_1 = 17 - R_3 \Rightarrow \begin{cases} (22 - R_3) \cdot I = 8 & (2') \\ (R_3 + 5) \cdot I = 4 & (3') \end{cases} \Rightarrow I = \frac{8}{22 - R_3}$$

$$\Rightarrow (R_3 + 5) \cdot \frac{8}{22 - R_3} = 4 \Rightarrow 2(R_3 + 5) = 22 - R_3 \Rightarrow 2R_3 + 10 = 22 - R_3 \Rightarrow 3R_3 = 12$$

$$\Rightarrow R_3 = 4 \Omega$$

$$\Rightarrow R_1 = 13 \Omega$$

$$\text{Tension aux bornes de la batterie: } I = \frac{8}{22 - 4} = \frac{8}{18} = \frac{4}{9}$$

$$\Rightarrow E = 22 \cdot \frac{4}{9} = \frac{88}{9} \approx 9,8 V$$