

Oscillations harmoniques: système masse-ressort et circuit L-C

résolution

jeudi, 31 décembre 2020 16:10

Masse-ressort

$$\ddot{z} = -\frac{k}{m} z$$

Conditions initiales:

$$t=0$$

$$\begin{cases} z(0) = x(0) - p_0 = A \\ \dot{z}(0) = 0 \end{cases}$$

Circuit L-C série

$$\ddot{q} = -\frac{1}{LC} q$$

Conditions initiales:

$$t=0$$

$$\begin{cases} q(0) = Q_0 \\ \dot{q}(0) = 0 \end{cases}$$

Forme générale: $\ddot{y} = -\alpha^2 y$

On remarque:

$$\begin{cases} \sin(x) = \cos(x) \\ \sin(x)' = \cos(x)' = -\sin(x) \end{cases}$$

On essaye $y(t) = B \sin(\omega t + \varphi)$

$$\dot{y} = B \omega \cos(\omega t + \varphi)$$

$$\ddot{y} = -B \omega^2 \sin(\omega t + \varphi)$$

$$\Rightarrow \underline{t=0} : y(0) = B \sin(\varphi) \xrightarrow{A \text{ (mécanique)}} B = A; \varphi = \frac{\pi}{2}$$
$$\xrightarrow{Q_0 \text{ (électro...)}} B = Q_0; \varphi = \frac{\pi}{2}$$

$$-B \omega^2 \sin(\omega t + \varphi) = -\alpha^2 B \sin(\omega t + \varphi)$$

$$\omega = \alpha \rightarrow \alpha = \sqrt{\frac{k}{m}}$$

$$\rightarrow \alpha = \sqrt{\frac{1}{LC}}$$

$$\Rightarrow \boxed{z(t) = A \sin\left(\sqrt{\frac{k}{m}} \cdot t + \frac{\pi}{2}\right) = x(t) - p_0}$$

$$\boxed{q(t) = Q_0 \sin\left(\sqrt{\frac{1}{LC}} \cdot t + \frac{\pi}{2}\right)}$$